

*Name – Arundhati Bandyopadhyay*

*Roll No. – 25300119058*

*Dept. – CSE*

1. One Flip Flop can store one bits of digital information.
2. A decoder has n outputs, so number of inputs will be  $\sqrt{n}$ .
3. 3-bit Johnson counter has modulus = 6
4. -20 in 1's complement form can be represented in binary as (101011)<sub>2</sub>.
5. 98 in Excess -3 code can be represented as (1100 1011)<sub>2</sub>.
6. A six-bit asynchronous counter has modulus = 64.
7. Number of clock pulses required to write 4-bit data synchronously into PISO register is 4.
8. The frequency of clock applied at the input of Mod-16 asynchronous counter is 32KHz. The frequency of waveform obtained at MSB output stage is 2KHz.

9. 16V is to be represented in digital word of 4-bits. The step of each interval is 1 and resolution of ADC is 1/16.
10. The minimum no. of NAND gates required to realise XOR gate is four.